

Jack Vincent Nicolas

CS 21 Project: MIPS Single Cycle Processor Extension

Video Documentation:

https://drive.google.com/file/d/1GKEDQeuFRxMr-8Q2W3YCq_26_PHu1NTW/view?usp=sharing

Documentation:

Pseudo-Instructions

1. Load Immediate (li)

- opcode is 0x11
- target register is in bits 20-16 (rt)
- rs (bits 25-21) are Xs (Don't cares - not necessarily zeroes)
- immediate field (bits 15-0) contain values to be stored to rt; when used in assembly language, assume value to be stored always no longer than 16 bits; logically- or zero-extend the 16-bit value to 32 when storing to register

The first module that had a change was the mips module. In this module, I simply changed the number of bits that the alucontrol will take from 3 bits ([2:0]) to 4 bits ([3:0]). The mips module contains the inputs clk, reset, a 32-bit instr and readdata. It has the outputs 32-bit pc, aluout, write data and an output of memwrite. It has local variables memtoreg, alusrc, regdst, regwrite, jump, pcsrc, zero and a 4-bit alu control. Under this are the controller and data path modules.

```

`timescale 1ns / 1ps
module mips(input logic      clk, reset,
            output logic [31:0] pc,
            input logic [31:0] instr,
            output logic      memwrite,
            output logic [31:0] aluout, writedata,
            input logic [31:0] readdata);

    logic      memtoreg, alusrc, regdst,
               regwrite, jump, pcsrc, zero;
    logic [3:0] alucontrol;

    controller c(instr[31:26], instr[5:0], zero,
                 memtoreg, memwrite, pcsrc,
                 alusrc, regdst, regwrite, jump,
                 alucontrol);
    datapath dp(clk, reset, memtoreg, pcsrc,
                alusrc, regdst, regwrite, jump,
                alucontrol,
                zero, pc, instr,
                aluout, writedata, readdata);
endmodule

```

The second module that I changed was the controller module. In this module, I changed the number of bits for the alucontrol from 3 bits to 4 bits. I also added the aluop to the input of aludec. It has the inputs 6-bit op and funct, and an input zero. It outputs memtoreg, memwrite, pcsrc, alusrc, regdst, regwrite, jump and the 4-bit alucontrol. It has local variables 2-bit aluop and a branch. Under this are the modules maindec and aludec.

```

`timescale 1ns / 1ps
module controller(input logic [5:0] op, funct,
                 input logic      zero,
                 output logic      memtoreg, memwrite,
                 output logic      pcsrc, alusrc,
                 output logic      regdst, regwrite,
                 output logic      jump,
                 output logic [3:0] alucontrol);

    logic [1:0] aluop;
    logic      branch;

    maindec md(op, memtoreg, memwrite, branch,
               alusrc, regdst, regwrite, jump, aluop);
    aludec ad(funct, aluop, op, alucontrol);

    assign pcsrc = branch & zero;
endmodule

```

The third module that I manipulated to add some instructions was the maindec module. The maindec module takes in as an input the opcode of the instruction. From the opcode, we will get the control signals that the instruction needs. We have the variable controls which contains 9 bits, wherein each bit denote a control signal. It has the arrangement regwrite, regdst, alusrc, branch, memwrite, memtoreg, jump and aluop.

```
`timescale 1ns / 1ps
module maindec(input logic [5:0] op,
               output logic memtoreg, memwrite,
               output logic branch, alusrc,
               output logic regdst, regwrite,
               output logic jump,
               output logic [1:0] aluop);

    logic [8:0] controls;

    assign {regwrite, regdst, alusrc, branch, memwrite,
           memtoreg, jump, aluop} = controls;
```

It is followed by an instruction case which checks the op and assigns the corresponding control signals for that instruction.

```
always_comb
case(op)
    6'b000000: controls <= 9'b110000010; // RTYPE
    6'b100011: controls <= 9'b101001000; // LW
    6'b101011: controls <= 9'b001010000; // SW
    6'b000100: controls <= 9'b000100001; // BEQ
    6'b001000: controls <= 9'b101000000; // ADDI
    6'b000010: controls <= 9'b000000100; // J
    6'b010001: controls <= 9'b101000000; // li (addi)
    default:   controls <= 9'bxxxxxxxx; // illegal op
endcase
endmodule
```

In this module, I added another case for the load immediate instruction. It checks the op for the case when it is 0x11 and assigns the control 9'b101000000 which is the same as in addi.

The fourth module that was changed was the datapath module. This module handles the logic which occurs inside a mips single cycle datapath. It takes in as input the clk, reset, memtoreg, pcsrc, alusrc, regdst, regwrite, jump, alucontrol, instr and readdata. Using the input, it outputs zero, pc, aluout and writedata.

It has local variables writetoreg, pcnext, pcnextbr, pcplus4, pcbranch, signimm, signimmsh, srca, srcb and result which are used for the operations inside the module.

```

`timescale 1ns / 1ps
module datapath(input logic clk, reset,
               input logic memtoreg, pcsrc,
               input logic alusrc, regdst,
               input logic regwrite, jump,
               input logic [3:0] alucontrol,
               output logic zero,
               output logic [31:0] pc,
               input logic [31:0] instr,
               output logic [31:0] aluout, writedata,
               input logic [31:0] readdata);

  logic [4:0] writereg;
  logic [31:0] pcnext, pcnextbr, pcplus4, pcbranch;
  logic [31:0] signimm, signimmsh;
  logic [31:0] srca, srcb;
  logic [31:0] result;

```

Under this, we have the next PC logic, register file logic and the ALU logic. The next PC logic is responsible for the address of the instructions being executed. The register file logic is responsible for the storage of the values that the instructions are executing. Finally, the alu logic is responsible for executing the instructions and returning the desired values.

```

// next PC logic
flop #(32) pcreg(clk, reset, pcnext, pc);
adder #(32) pcadd1(pc, 32'b100, 'b0, pcplus4); //So we adjust this to use
the more complex adder; wmt-modification
s12      immsh(signimm, signimmsh);
adder #(32) pcadd2(pcplus4, signimmsh, 'b0, pcbranch); //See comment above
mux2 #(32) pcbrmux(pcplus4, pcbranch, pcsrc, pcnextbr);
mux2 #(32) pcmux(pcnextbr, {pcplus4[31:28],
                           instr[25:0], 2'b00}, jump, pcnext);

// register file logic
regfile   rf(clk, regwrite, instr[25:21], instr[20:16],
            writereg, result, srca, writedata);
mux2 #(5) wrmux(instr[20:16], instr[15:11],
               regdst, writereg);
mux2 #(32) resmux(aluout, readdata, memtoreg, result);
signext    se(instr[15:0], signimm);

// ALU logic
mux2 #(32) srcbmux(writedata, signimm, alusrc, srcb);
alu        alu(srca, srcb, alucontrol, aluout, zero);
endmodule

```

In this module, I simply changed the number of bits that the alucontrol will take from 3 bits to 4 bits, which is highlighted above.

The fifth module that I changed and added some instructions was the alu module. This is where the main operation happens. We have 32-bit inputs a and b, and a 4-bit input called alucontrol. This

then outputs, a 32-bit output result and an output zero. We have some local variables here, a 32-bit `condinvb`, `sum` and `mask`. The `condinvb` checks `alucontrol[3]` (leftmost bit) if it will turn input `b` to negative. The `sum` adds input `a` and `b`. The `mask` is assigned a hex value of `'h0000FFFF`. Under this we have cases for `alucontrol[2:0]` (the remaining bits after the leftmost bit is discarded), it performs the operations depending on the last 3 bits of the `alucontrol`. If it is `'b000`, it performs an AND operation, when it is `'b001`, it performs an OR operation, when it is `'b010`, it returns the `sum`, when it is `'b011`, it returns `sum[31]` and finally if it is `'b100`, it performs the AND operation between `mask` and `b`. The and between `mask` and `b` returns the zero-extended immediate field of the MIPS instruction.

```
module alu(input logic [31:0] a, b,
          input logic [3:0] alucontrol,
          output logic [31:0] result,
          output logic zero);

    logic [31:0] condinvb, sum, mask;

    assign condinvb = alucontrol[3] ? ~b : b;
    assign sum = a + condinvb + alucontrol[3];
    assign mask = 'h0000FFFF;

    always_comb
        case (alucontrol[2:0])
            3'b000: result = a & b;
            3'b001: result = a | b;
            3'b010: result = sum;
            3'b011: result = sum[31];
            3'b100: result = mask & b;
        endcase

    assign zero = (result == 32'b0);
endmodule
```

The last module that we changed and added some instructions to is the `aludec` module. In this module, we have the inputs 6-bit `funct`, 2-bit `aluop` and we added the 6-bit `op` as a change from the original module, then we have the 4-bit `alucontrol` for the output.

Under this, we have the case for the `aluop`. If the `aluop` is `'b00`, I placed another case inside wherein if it has an opcode of `6'b010001`, then it has an `alucontrol` of `4'b0100` which is used for the load immediate instruction, else it has an `alucontrol` of `4'b0010`. If it has an opcode `2'b01`, then it has an `alucontrol` of `4'b0010`. In the case of R-type instructions, it will be assigned to the default case wherein it checks the `funct` value of the instruction. If it has the `funct` `6'b100000`, then it has an `alucontrol` `4'b0010` for add. If it has the `funct` `6'b100010`, then it has an `alucontrol` `4'b1010` for sub. If it has the `funct` `6'b100100`, then it has an `alucontrol` `4'b0000` for and. If it has the `funct` `6'b100101`, then it has an `alucontrol` `4'b0001` for or. If it has the `funct` `6'b101010`, then it has an `alucontrol` `4'b1011` for slt. And in default, it has `alucontrol` `4'bxxxx`.


```


`timescale 1ns / 1ps
module aludec(input logic [5:0] funct,
              input logic [1:0] aluop,
              input logic [5:0] op,
              output logic [3:0] alucontrol);

  always_comb
  case(aluop)
    2'b00: case(op)
      6'b010001: alucontrol <= 4'b0100; // li
      default: alucontrol <= 4'b0010; // add (for lw/sw/addi)
    endcase
    2'b01: alucontrol <= 4'b0110; // sub (for beq)
    default: case(funct) // R-type instructions
      6'b100000: alucontrol <= 4'b0010; // add
      6'b100010: alucontrol <= 4'b1010; // sub
      6'b100100: alucontrol <= 4'b0000; // and
      6'b100101: alucontrol <= 4'b0001; // or
      6'b101010: alucontrol <= 4'b1011; // slt
      default: alucontrol <= 4'bxxxx; // ???
    endcase
  endcase
endmodule


```

Schematic Diagram

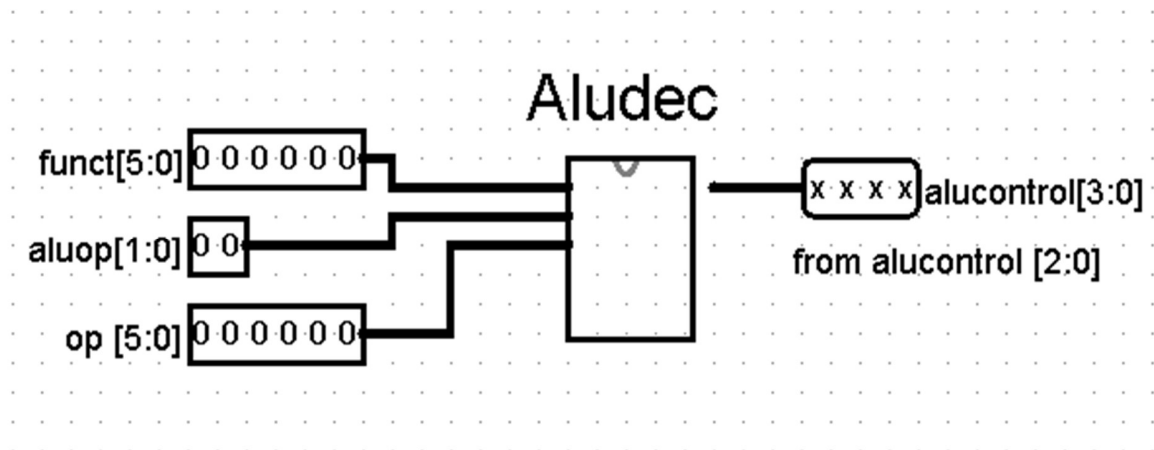In the aludec, the number of bits for the alucontrol was changed, so this was depicted in the diagram below.



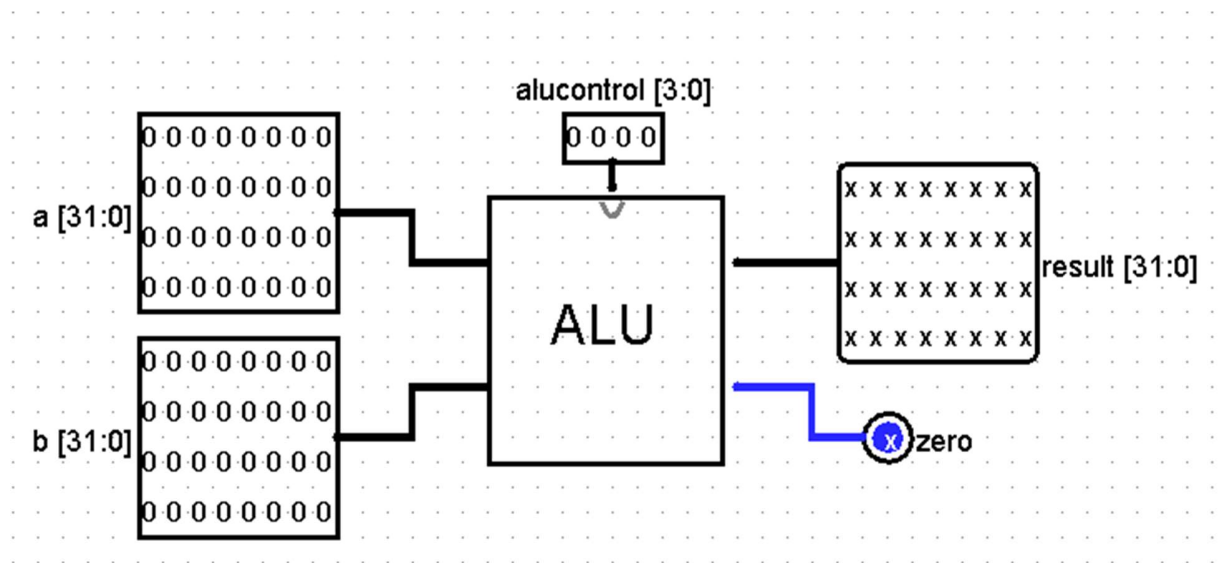In the ALU, the input of alucontrol was changed from 3 bits top 4 bits, so this was depicted in the diagram below.



How the instructions were tested?


First Testcase: Checking if the li works as intended.

HEX CODE	MIPS Instruction
4401C000	li \$1 C000
440200DE	li \$2 00DE
00220820	add \$1 \$1 \$2

The result should be 0xC0DE



We managed to get the right output.

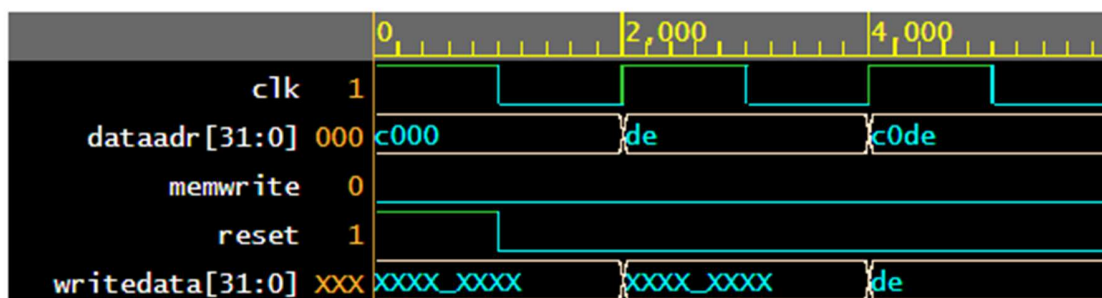

Second Testcase: Checking if the li works as intended even if the rs part of the instruction isn't 0. (Simply put, rs = XXXXX)

HEX CODE	MIPS Instruction
4421C000	li \$1 0xC000
448200DE	li \$2 0x00DE
00220820	add \$1 \$1 \$2

Again, the result must be 0xC0DE

A screenshot of the IDE's editor window. The title bar shows 'design.sv' and 'memfile.mem'. The editor content shows three lines of memory addresses: 1 4421C000, 2 448200DE, and 3 00220820|.

We still managed to get the right output.




Third testcase: I utilized the memfile for lab 12, replacing the `addi $register $0 0XXXXX` to `li $register 0XXXXX`. This shows that it works with other instructions as well as show that it works with the previous outputs.

[illegible]

00210820	add \$1 \$1 \$1
00210820	add \$1 \$1 \$1
00210820	add \$1 \$1 \$1
00210820	add \$1 \$1 \$1
00210820	add \$1 \$1 \$1
440200B0	li \$2 0x00B0
00421820	add \$2 \$2 \$2
00631820	add \$2 \$2 \$2
00631820	add \$2 \$2 \$2
00631820	add \$2 \$2 \$2
00631820	add \$2 \$2 \$2
00631820	add \$2 \$2 \$2
00631820	add \$2 \$2 \$2
00631820	add \$2 \$2 \$2
00232020	add \$4 \$1 \$3
44050010	li \$5 0x0010
ACA40000	sw \$4 (\$5)

The stored output should be 0xBBAAB0B0

We managed to get the right output.

 

Note: To revert to EPWave opening in a new browser window, set that option on your user page.